

IOWA STATE UNIVERSITY

ECpE Department

EE 303 Energy Systems and Power Electronics

Introduction to Power Basics

GRA: Prashant Tiwari

Advisor: Dr. Zhaoyu Wang

1113 Coover Hall, Ames, IA

wzy@iastate.edu


IOWA STATE UNIVERSITY

Phasor

Complex Number: $Z = a + jb$

- Exponential Form: $Z = |Z| \cdot e^{j\theta}$;
where, $|Z| = \sqrt{a^2 + b^2}$,
 $\theta = \arctan \frac{b}{a}$,
 $e^{j\theta} = \cos \theta + j \sin \theta$
- Polar Form: $Z = |Z| \angle \theta$
- Rectangular Form: $Z = |Z| \cos \theta + j|Z| \sin \theta$

Conjugation: $Z^* = a - jb$

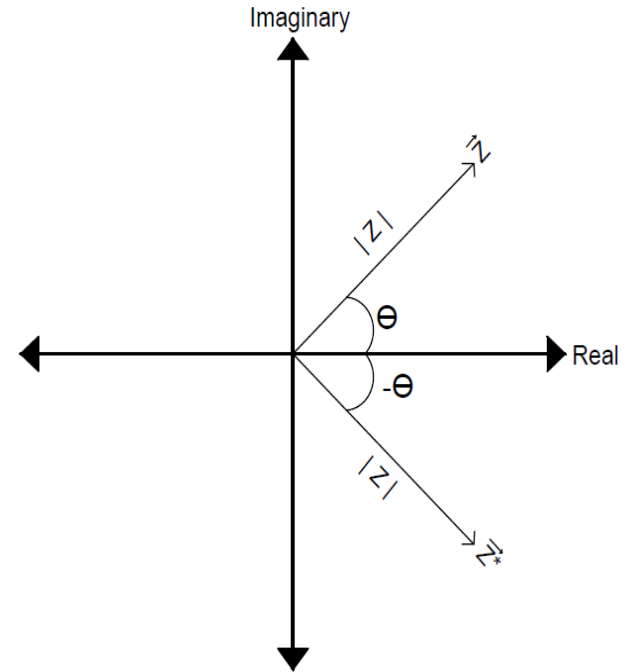


Mathematical Operations

$$\begin{aligned}Z_1 + Z_2 &= a_1 + jb_1 + a_2 + jb_2 \\ &= (a_1 + a_2) + j(b_1 + b_2)\end{aligned}$$

$$\begin{aligned}Z_1 \cdot Z_2 &= (a_1 + jb_1) \cdot (a_2 + jb_2) \\ &= (a_1 a_2 - b_1 b_2) + j(a_1 b_2 + b_1 a_2) \\ &= |Z_1| e^{j\theta_1} \cdot |Z_2| e^{j\theta_2} = |Z_1| |Z_2| e^{j(\theta_1 + \theta_2)}\end{aligned}$$

Time Domain

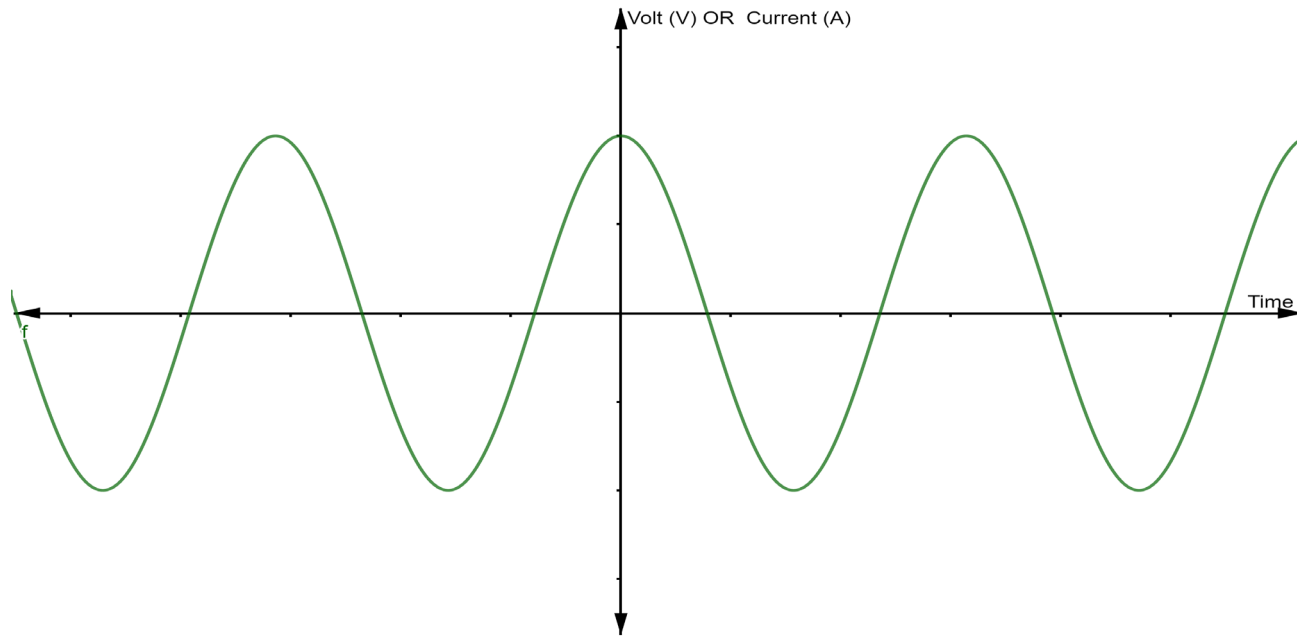

$$V(t) = V_{max} \cos(\omega t + \theta_V)$$

$$I(t) = I_{max} \cos(\omega t + \theta_I) ; \text{ where,}$$

$$\omega = 2\pi f; f \text{ is } 60\text{Hz}$$

Time Domain VS Phasor Domain

Objective: Phasor Domain Analysis for simplifying calculations

Assumption:

- Constant frequency system
- Sine Wave

Time Domain Representation

- We discussed in Lecture 1, the Time domain representation of voltage and current are,

$$V(t) = V_{max} \cos(\omega t + \theta_V)$$

$$I(t) = I_{max} \cos(\omega t + \theta_I)$$

- Root Mean Square (RMS) of a sine signal is,

$$|V| = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt} = \frac{V_{max}}{\sqrt{2}}; \text{ where } T = \frac{1}{f}$$

Contd...

- $V(t) = \sqrt{2} |V| \cos(\omega t + \theta_V)$
- $I(t) = \sqrt{2} |I| \cos(\omega t + \theta_I)$ (i)
- $V(t) = \sqrt{2} |V| \operatorname{Re} [e^{j(\omega t + \theta_V)}]$ (ii)
- $I(t) = \sqrt{2} |I| \operatorname{Re} [e^{j(\omega t + \theta_I)}]$

Note: [For conversion of equation (i) to (ii)]

$$\text{As, } e^{j\theta} = \cos \theta + j \sin \theta$$

$$\therefore e^{j(\omega t + \theta_V)} = \underbrace{\cos(\omega t + \theta_V)}_{\text{Real Part}} + j \underbrace{\sin(\omega t + \theta_V)}_{\text{Imaginary Part}}$$

Phasor Domain Representation

Voltage and Current can be represented in phasor domain as,

- $V = |V|e^{j\theta_V} = |V|\angle\theta_V = |V|\cos\theta_V + j|V|\sin\theta_V$
- $I = \underbrace{|I|e^{j\theta_I}}_{\text{Exponential}} = \underbrace{|I|\angle\theta_I}_{\text{Polar}} = \underbrace{|I|\cos\theta_I + j|I|\sin\theta_I}_{\text{Rectangular}}$

Representation of Electrical Components

Component	Time Domain	Phasor Domain
Resistor	$V(t) = R \cdot i(t)$	$V = R \cdot I$
Inductor	$V(t) = L \cdot \frac{d i(t)}{dt}$	$V = j\omega L \cdot I$
Capacitor	$V(t) = \frac{1}{C} \int_0^t i(t) dt + V(0)$	$V = \frac{1}{j\omega C} \cdot I$

Impedance

‘Z’ denotes the impedance.

Mathematically,

$$Z = R + jX, \text{ where } R = \text{resistance and}$$

$$X = \text{reactance}$$

$$= R + j(X_L - X_C)$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Note:

Here, $X_L = \omega L$ and is called ‘Inductive Impedance’

and, $X_C = \frac{1}{\omega C}$ and is called ‘Capacitive Impedance’

Contd..

Expression of Z in polar form.


$$\text{As, } Z = R + jX$$

$$\text{In Polar Form, } Z = |Z| \angle \phi ; \text{ where, } |Z| = \sqrt{R^2 + X^2}$$
$$\text{and } \phi = \arctan\left(\frac{X}{R}\right)$$

- The reciprocal of Impedance is termed as admittance.

$$\text{i.e. } Y = \frac{1}{Z}$$

Example 1: Find $i(t)$

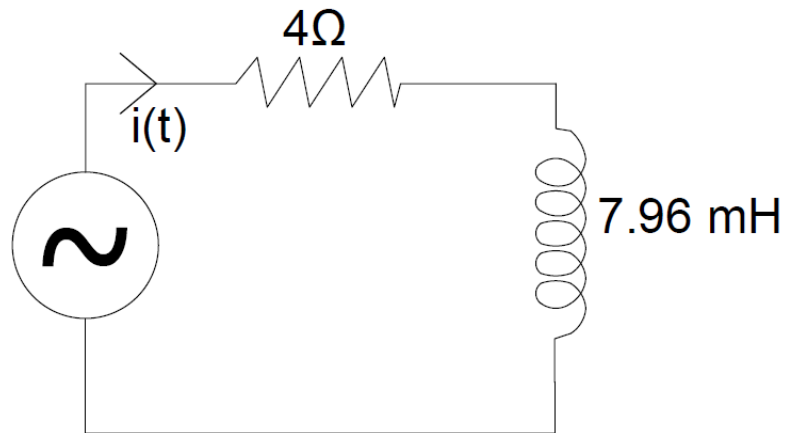

The voltage source in the figure shown is defined as $V(t)$ where,

$$V(t) = \sqrt{2} 100 \cos(\omega t + 30)$$

Find $i(t)$.

Solution

Given,

$$R = 4\Omega,$$

$$X = \omega L = 2\pi fL = 3$$


$$\therefore Z = 4 + j3$$

$$|Z| = \sqrt{4^2 + 3^2} = 5 \text{ and}$$

$$\phi = \arctan\left(\frac{3}{4}\right) = 36.9^\circ$$

$$\text{Now, } I = \frac{V}{Z} = \frac{100\angle 30}{5\angle 36.9} = 20\angle -6.9^\circ \text{ A}$$
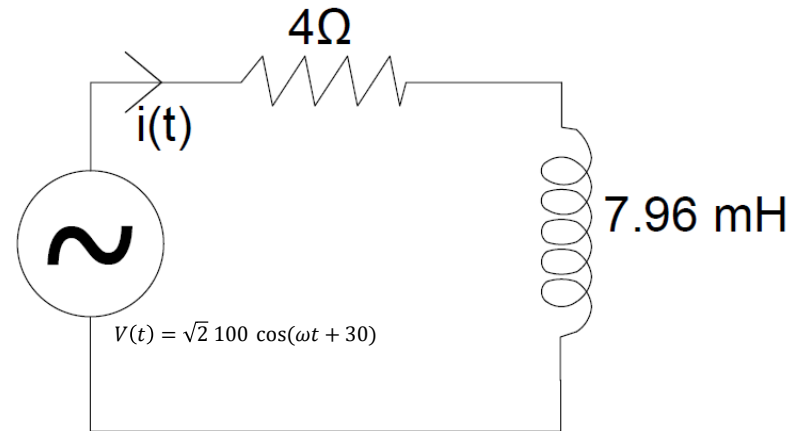
$$\therefore i(t) = 20\sqrt{2} \cos(\omega t - 6.9)$$



Complex Power

$$\text{Power}(t) = V(t) \cdot I(t) \quad \text{where, } V(t) = V_{max} \cos(\omega t + \theta_V) \\ I(t) = I_{max} \cos(\omega t + \theta_I)$$

$$\left[\because \cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)] \right]$$

$$\Rightarrow \text{power}(t) = \frac{1}{2} V_{max} I_{max} [\cos(\theta_V - \theta_I) + \cos(2\omega t + \theta_V + \theta_I)]$$

$$\Rightarrow \text{power}(t) = \frac{1}{2} V_{max} I_{max} [\cos(\theta_V - \theta_I) + \cos(2(\omega t + \theta_V) - (\theta_V - \theta_I))]$$

$$\Rightarrow \text{power}(t) = \frac{1}{2} V_{max} I_{max} \cos(\theta_V - \theta_I) \{1 + \cos[2(\omega t + \theta_V)]\} \quad \left[\because \cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta \right] \\ + \frac{1}{2} V_{max} I_{max} \sin(\theta_V - \theta_I) \sin[2(\omega t + \theta_V)]$$


Contd...

- Average Power = $\frac{1}{2} \int_0^T power(t) dt$
= $\frac{1}{2} V_{max} I_{max} \cos(\theta_V - \theta_I)$
= $|V||I| \underbrace{\cos(\theta_V - \theta_I)}_{\text{Power factor Angle } (\phi)}$
- ✓ Power factor (pf) = $\cos \phi$ [pf lies between 0 and 1]
- ✓ Average power is also referred as active power.


Contd...

Note:

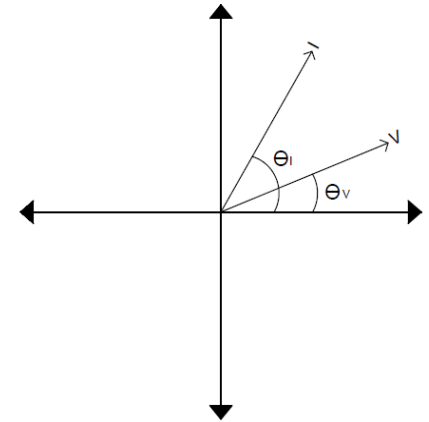1. If current leads voltage, $\theta_V - \theta_I < 0$
then pf is leading.



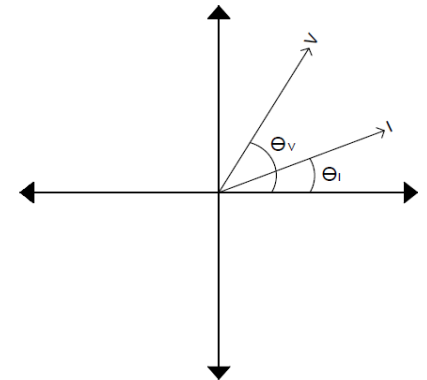2. If current lags voltage, $\theta_V - \theta_I > 0$
then pf is lagging.



Contd...

- Active Power (P) = $|V||I| \cos(\theta_V - \theta_I)$ (Watts)
- Reactive Power (Q) = $|V||I| \sin(\theta_V - \theta_I)$ (VAr)

Complex Power, $S = P + jQ$ (Unit of S is usually VA, kVA)

$$S = |V||I| [\cos(\theta_V - \theta_I) + j \sin(\theta_V - \theta_I)]$$

$$= V \cdot I^*$$

$$= |V| \angle \theta_V \cdot |I| \angle -\theta_I$$

$$= |V||I| \angle (\theta_V - \theta_I)$$

Contd...

- Magnitude of Apparent Power:


$$|S| = |V| \cdot |I| = \sqrt{P^2 + Q^2}$$

The real power, reactive power and apparent power can be represented as shown in the figure. The figure is called power triangle.

From Power Triangle, we can get,

$$P = S \cdot \cos \phi$$

$$Q = S \cdot \sin \phi = \pm S \sqrt{1 - pf^2}$$

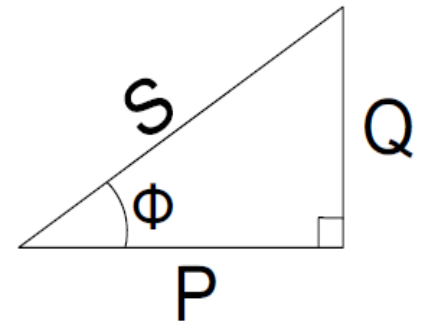

Example 2:

A load draws 100kW with leading pf of 0.85. What is ϕ , Q and S?

Solution:

Contd...

Q. A load draws 100kW with leading pf of 0.85. What is ϕ , Q and S?

Solution:

- $\Phi = -\cos^{-1}(0.85) = -31.8^\circ$
- Apparent Power (S) = $\frac{P}{\cos \Phi} = 117.6 \text{ Kva}$
- Reactive Power (Q) = $S \cdot \sin \Phi = -62 \text{ kVAr}$
- Complex Power (S) = $P + jQ = 100 - j62$

Review

- Voltage Phasor: $V = |V|\angle\theta_V = |V|\cos\theta_V + j|V|\sin\theta_V$

- Complex Power:

$$S = |V||I|[\cos(\theta_V - \theta_I) + j\sin(\theta_V - \theta_I)]$$

$$= P + jQ$$

$$= |V||I|^*$$

P is Real Power/ Active Power, Units – W, kW, μ W


Q is Reactive Power, Units – VAR, kVAR, μ VAR

S is Complex Power, Units – VA, kVA, Mva


Contd...

- Power factor Angle: $\phi = \theta_V - \theta_I$
- Power factor (pf): $\cos \phi$ (value ranges from 0 to 1)
- Leading pf: current angle leads voltage angle ($\theta_V - \theta_I < 0$).
- Lagging pf: current angle lags voltage angle ($\theta_V - \theta_I > 0$).

39 – Bus Test System

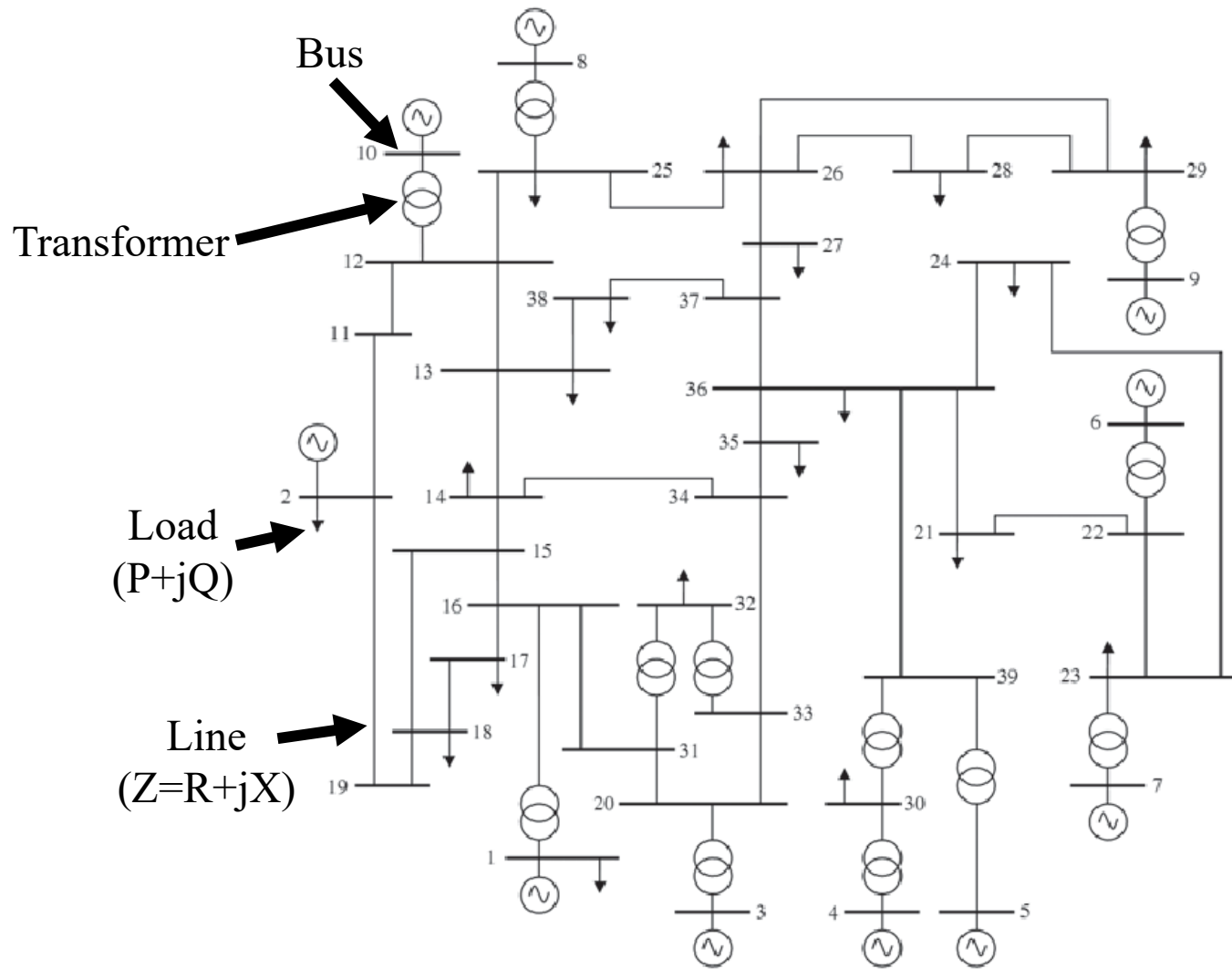


118 – Bus Test System

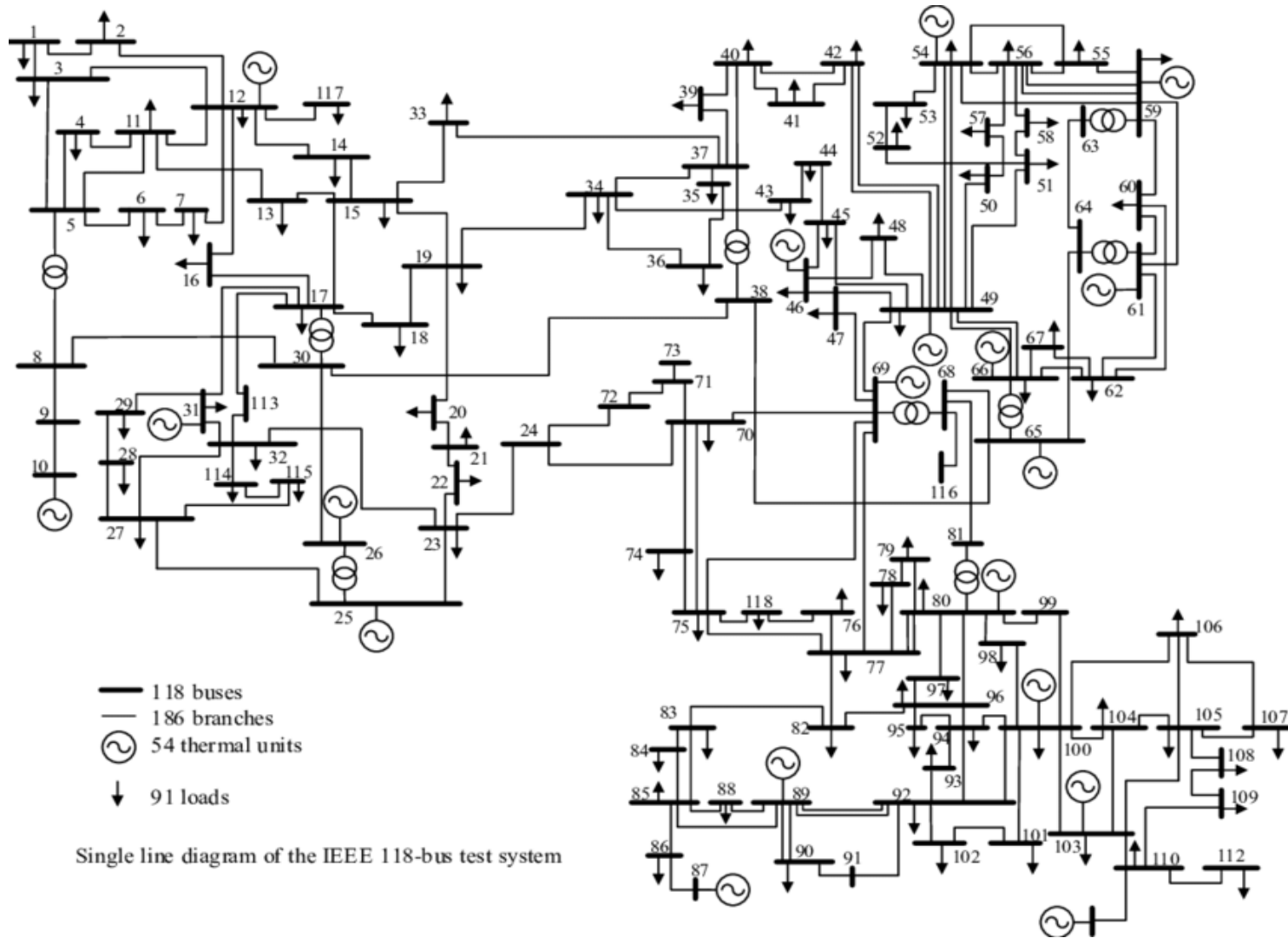

Example 1:

The voltage source in the figure shown is defined as $V(t)$ where,

$$V(t) = 100\angle 30^\circ$$

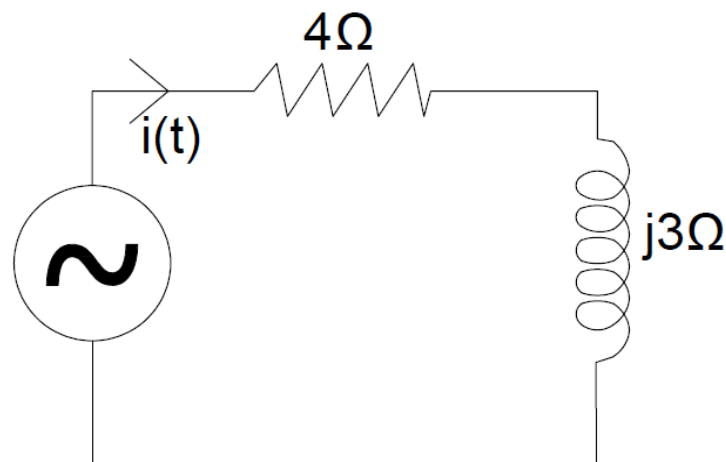


Solution

We know,

$$I = \frac{V}{Z} = \frac{100\angle 30^\circ}{4+j3} = 20\angle -6.9^\circ \text{ A}$$

$$S = V \cdot I^* = 100\angle 30^\circ * 20\angle 6.9^\circ = 2000\angle 36.9^\circ \\ = 2000\angle 36.9^\circ \text{ VA} = 1600 \text{ W} + j1200 \text{ VAr}$$

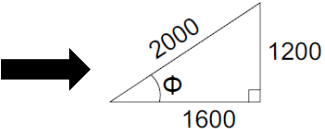
$$\phi = \arctan\left(\frac{1200}{1600}\right) = 36.9^\circ$$


$$\cos \phi = pf = 0.8 \text{ (lagging)}$$

Now,

$$S_R = V_R \cdot I^* = 4 * 20\angle -6.9^\circ * 20\angle 6.9^\circ \\ = 1600 \text{ W} \longrightarrow |I|^2 \cdot R$$

$$S_X = V_L \cdot I^* = 3j * 20\angle -6.9^\circ * 20\angle 6.9^\circ \\ = 1200 \text{ VAr} \longrightarrow |I|^2 \cdot X$$

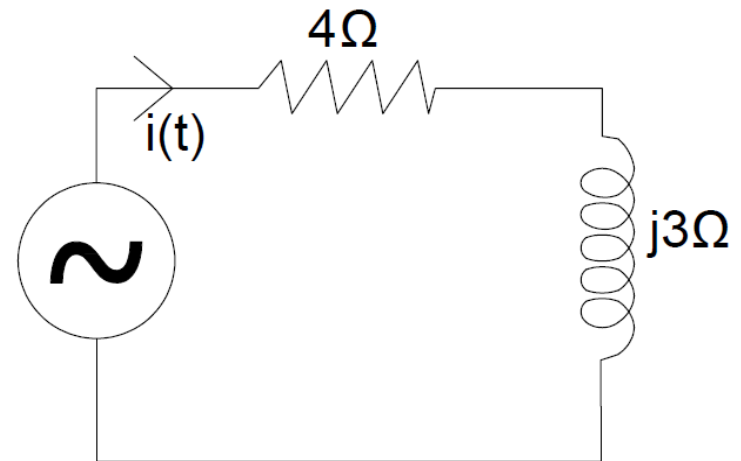

Contd...

Notes:

- Inductors only **consume** reactive power.

$$Q_{inductor} = |I_{inductor}|^2 \cdot X_L$$

$$\text{where, } X_L = j\omega L$$


- Capacitors only **generate** reactive power.

$$Q_{capacitor} = |I_{capacitor}|^2 \cdot X_C$$

$$\text{where, } X_C = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

Example 2:

Assume a load 100 kVA with $\text{pf}=0.8$ lagging, where as correct pf is 0.95 lagging. Find the value of reactive power that must be injected to maintain the correct pf .

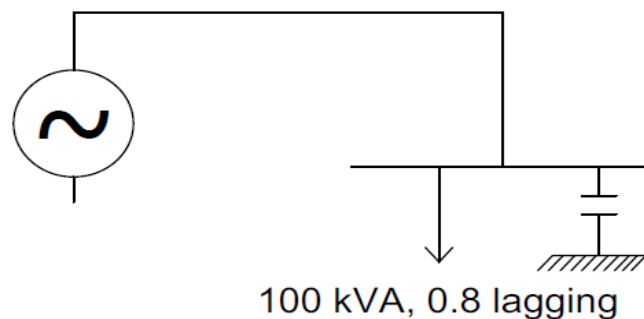

Example 2:

Assume a load 100 kVA with $\text{pf}=0.8$ lagging, where as correct pf is 0.95 lagging. Find the value of reactive power that must be injected to maintain the correct pf .




$$S = P+jQ = 80+j60$$

$$\phi = \text{arc cos } 0.8 = 36.9^\circ$$

$$\phi = \text{arc cos } 0.95 = 18.2^\circ$$

$$\tan 18.2^\circ = \frac{60 - Q_{\text{cap}}}{80}$$

$$Q_{\text{cap}} = 33.7 \text{ kVAR}$$

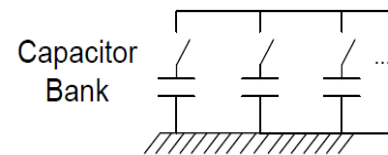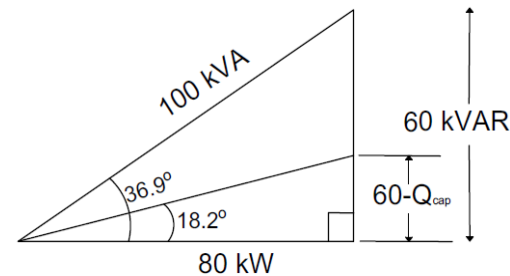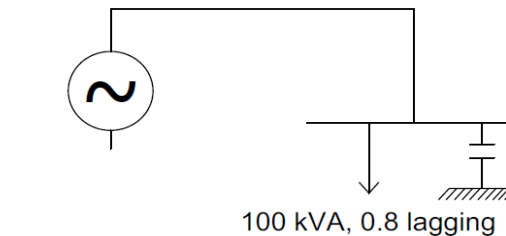

Thank You!