

IOWA STATE UNIVERSITY

ECpE Department

## EE 303 Energy Systems and Power Electronics

### Per Unit Analysis

GRA: Prashant Tiwari

Advisor: Dr. Zhaoyu Wang

1113 Coover Hall, Ames, IA

wzy@iastate.edu

IOWA STATE UNIVERSITY

# Per Unit Analysis

## Motivation:

It would be difficult to continuously refer impedance to the different sides of transformer.

Mathematically,

$$\text{Quantity in Per Unit} = \frac{\text{Actual Quantity}}{\text{Base value of the Quantity}}$$

# Normalization of all variables

$S, V, Z \text{ & } I$       (*Note: Ohms law still holds*)

- Pick  $S_B$  &  $V_B$ , and calculate  $I_B$  &  $Z_B$

$$S_B = V_B \cdot I_B^*$$


$$I_B = \left( \frac{S_B}{V_B} \right)^* = \frac{S_B}{V_B}$$

(*Note: Base values are real numbers*)

$$Z_B = \frac{(V_B)^2}{S_B}$$

- $S_B$  is for the entire system.
- $V_B$  is for each different voltage level.
- Base voltages are related by transformer turns ratio

# Contd...

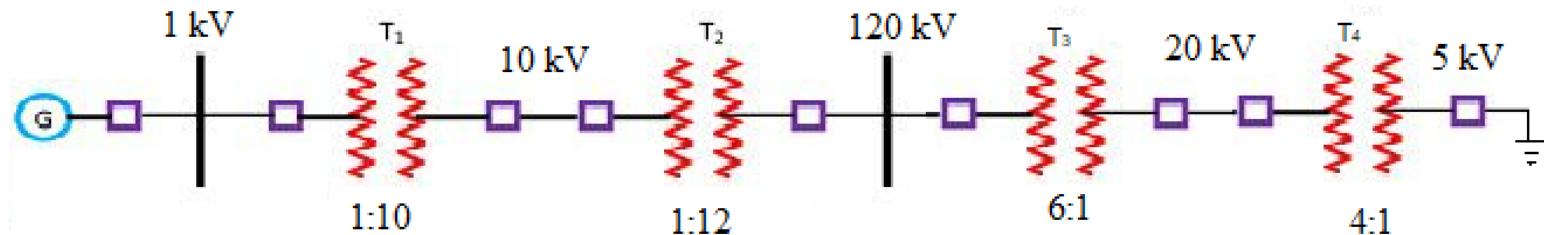

For a single-phase system:

- Step 1: Pick a single-phase **base power** for the entire system  $S_B$ .
- Step 2: Pick a **base voltage** for each different voltage level,  $V_B$ 
  - Base voltages are related by turns ratios.
  - voltages are line-to-neutral.
- Step 3: Calculate **base impedance**,  $Z_B = \frac{(V_B)^2}{S_B}$ .
- Step 4: Calculate **base current**,  $I_B = \frac{V_B}{S_B}$

# Contd...

- Step 5. Convert actual values to per unit (p.u.)

## Notes:

- 1) Base values are real numbers. Per unit conversion only affects magnitude, not angle.
- 2) Per unit quantities no longer have units.

## Contd...

$$V_{p.u} = \frac{V}{V_B};$$

$$P_{p.u} = \frac{P}{S_B};$$

$$S_{p.u} = \frac{S}{S_B};$$

$$Q_{p.u} = \frac{Q}{S_B};$$


$$I_{p.u} = \frac{I}{I_B};$$

$$R_{p.u} = \frac{R}{Z_B};$$

$$Z_{p.u} = \frac{Z}{Z_B};$$

$$X_{p.u} = \frac{X}{Z_B};$$
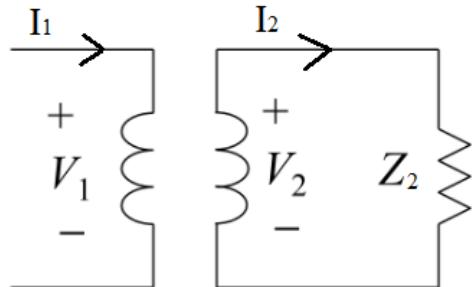
# Per Unit Values of Primary and Secondary Side of a Transformer are EQUAL



$N_1 : N_2$

$$a = \frac{N_1}{N_2}$$

$$V_2 = n \cdot V_1 = \frac{V_1}{a}$$

$$n = \frac{N_2}{N_1}$$

$$I_2 = \frac{I_1}{n} = a \cdot I_1$$


Transformation  
Ratio

Real Values

## Choose Base Values:

- $S_B$
- $V_{1B}$     &     $V_{2B} = \frac{V_{1B}}{a} = n \cdot V_{1B}$
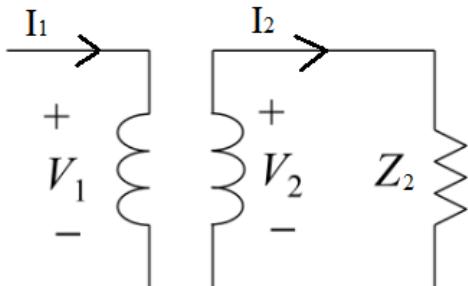
# Per Unit Values of Primary and Secondary Side of a Transformer are EQUAL



$N_1 : N_2$


Choose Base Values:

- $S_B$
- $V_{1B}$  &  $V_{2B} = \frac{V_{1B}}{a} = n \cdot V_{1B}$

$$V_{2,pu} = \frac{V_2}{V_{2B}} = \frac{n \cdot V_1}{n \cdot V_{1B}} = \frac{V_1}{V_{1B}} = V_{1,pu}$$

$$I_{2,pu} = \frac{I_2}{I_{2B}} = \frac{I_2}{\frac{S_B}{V_{2B}}} = \frac{V_{2B} \cdot I_2}{S_B} = \frac{n \cdot V_{1B} \cdot I_2}{S_B} = \frac{n \cdot V_{1B} \cdot a \cdot I_1}{S_B} = \frac{V_{1B} \cdot I_1}{S_B} = \frac{I_1}{\frac{S_B}{V_{1B}}} = \frac{I_1}{I_{1B}} = I_{1,pu}$$
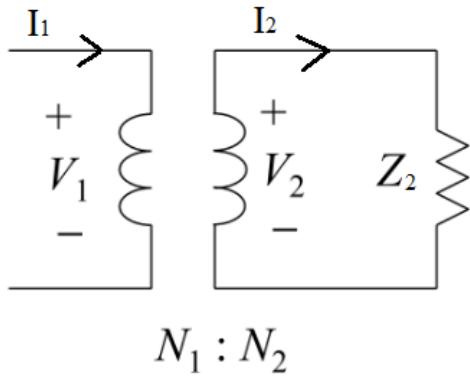
# Per Unit Values of Primary and Secondary Side of a Transformer are EQUAL



Choose Base Values:


- $S_B$
- $V_{1B}$  &  $V_{2B} = \frac{V_{1B}}{a} = n \cdot V_{1B}$

$$Z_{2B} = \frac{V_{2B}^2}{S_B} = \frac{n^2 \cdot V_{1B}^2}{S_B} = n^2 \cdot Z_{1B}$$

$$Z_{2; p.u} = \frac{Z_2}{Z_{2B}} = \frac{n^2 \cdot z_e}{n^2 \cdot Z_{1B}} = \frac{z_e}{Z_{1B}} = z_e; p.u.$$
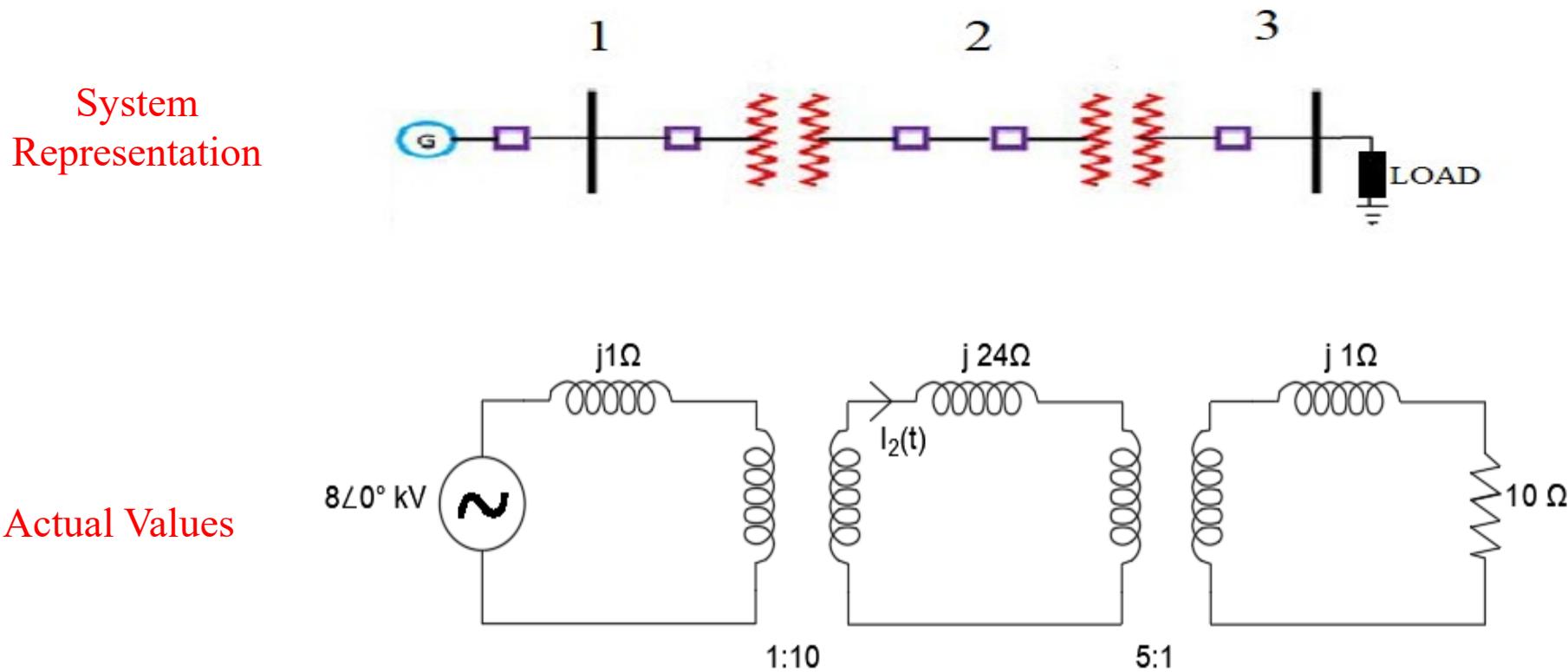
# Example 1

Q. Solve for the current, load voltage & load power in the following circuit using P.U. analysis with an  $S_B = 100\text{MVA}$  and base voltage of  $V_{B1} = 8\text{kV}$ ,  $V_{B2} = 80\text{kV}$ , and  $V_{B3} = 16\text{kV}$ .



# Example 1: Solution


$$V_{B1} = 8\text{kV}; \quad V_{B2} = 80\text{kV}; \quad V_{B3} = 16\text{kV}$$

$$Z_{B1} = \frac{(8 \text{ kV})^2}{100\text{MVA}} = 0.64\Omega.$$

$$Z_{B2} = \frac{(80 \text{ kV})^2}{100\text{MVA}} = 64\Omega.$$

$$Z_{B3} = \frac{(16 \text{ kV})^2}{100\text{MVA}} = 2.56\Omega.$$

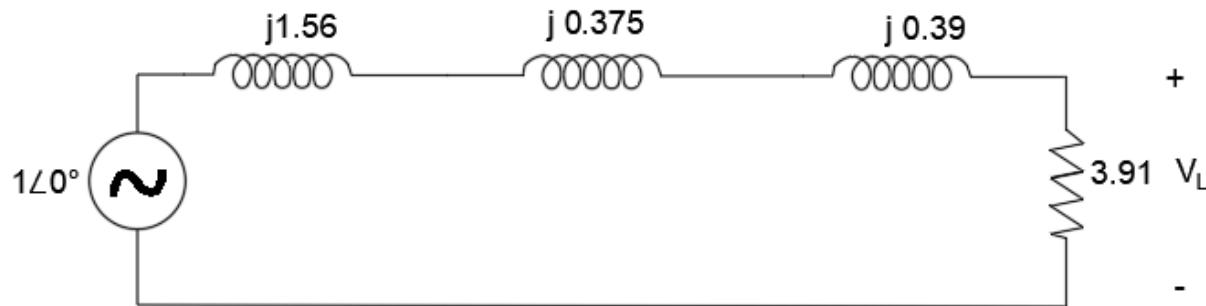Therefore, we can convert the actual values diagram in p.u. diagram.



## Contd...

$$I = \frac{1\angle 0^\circ}{3.91+j2.327} = 0.22\angle -30.8^\circ p.u.$$

$$V_L = 1\angle 0^\circ - 0.22\angle(-30.8^\circ) \times j2.327 = 0.859\angle -30.8^\circ p.u.$$

$$S_L = V_L \cdot I_L^* = 0.189 p.u.$$

$$S_G = V_G \cdot I_G^* = 1\angle 0^\circ * 0.22 \angle 30.8^\circ = 0.22\angle 30.8^\circ p.u$$

# Contd...

**Convert back to actual values.**

$$V_L^{actual} = 0.859 \angle (-30.8^\circ) \times 16kV = 13.7 \angle (-30.8^\circ) kV$$

$$S_L^{actual} = 0.189 \angle 0^\circ \times 100MVA = 18.9 \angle 0^\circ MVA$$

$$S_G^{actual} = 0.22 \angle 30.8^\circ \times 100MVA = 22 \angle 30.8^\circ MVA$$

$$I_{2B} = \frac{100MVA}{80kV} = 1250 A$$


$$I_2^{actual} = 0.22 \angle -30.8^\circ \times 1250 A = 275 \angle -30.8^\circ A$$

# Three- Phase Per Unit Analysis

- Step 1: Pick a Three-phase **base power** for the entire system  $S_B^{3\phi}$
- Step 2: Pick a **base voltage** for each different voltage level,  $V_{B, LL}$ 
  - L-L Base  $V_{B,LL}$
  - L-N Base  $V_{B,LL/\sqrt{3}}$
- Step 3: Calculate **Base Impedance**,  $Z_B = \frac{\left(\frac{V_{B,LL}}{\sqrt{3}}\right)^2}{\left(\frac{S_B^{3\phi}}{3}\right)} = \frac{V_{B,LL}^2}{S_B^{3\phi}}$
- Step 4: Calculate **Base current**,  $I_B^{3\phi} = \frac{\frac{S_B^{3\phi}}{3}}{\frac{V_{B,LL}}{\sqrt{3}}} = \frac{S_B^{3\phi}}{\sqrt{3}V_{B,LL}}$
- Step 5: Convert actual values to p.u.

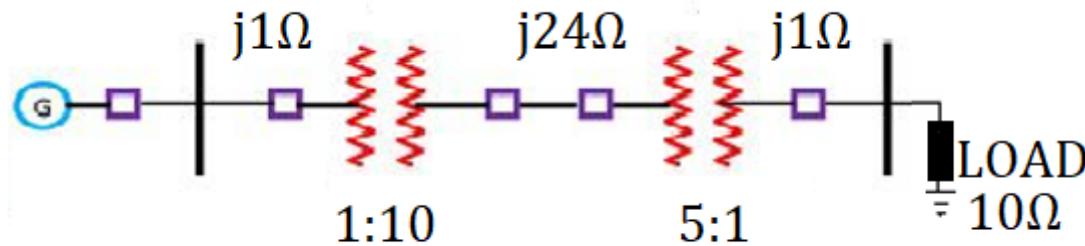
## Example 2:

Solve for the current, load voltage and load power in the previous circuit, assuming a 3 $\phi$  base power of 300 MVA, and line to line base voltages of 13.8 kV, 138 kV and 27.6 kV (square root of 3 larger than the 1 $\phi$  example voltages). Also assume the generator is Y-connected so its line-to-line voltage is 13.8 kV.



$$V_{B1} = 13.8 \text{ kV}, V_{B2} = 138 \text{ kV} \text{ and } V_{B3} = 27.6 \text{ kV}$$

## Example 2: Solution

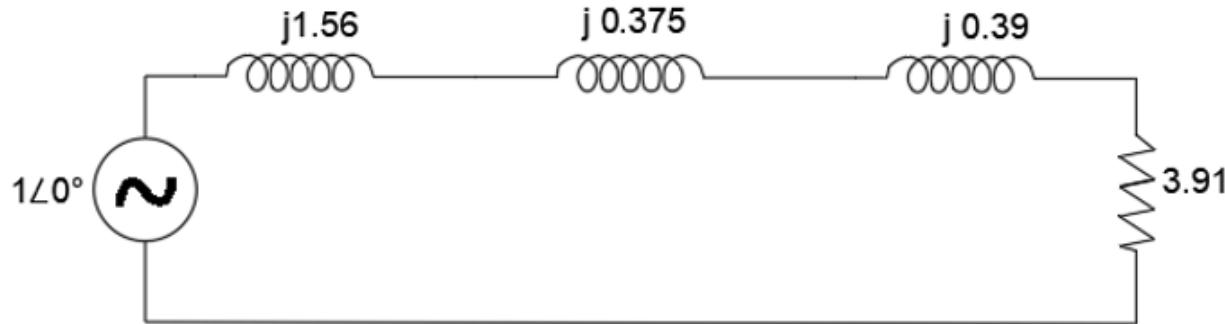

Convert to per unit as before. Note the system is exactly the same as example 1!

$$I = \frac{1.0\angle 0^\circ}{3.91+j2.327} = 0.22\angle -30.8^\circ \text{ p.u. (not amps)}$$

$$V_L = 1.0\angle 0^\circ - 0.22\angle -30.8^\circ \times 2.327\angle 90^\circ = 0.859\angle -30.8^\circ \text{ p.u.}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$

# Contd...

$$S_G = 1.0 \angle 0^\circ \times 0.22 \angle 30.8^\circ = 0.22 \angle 30.8^\circ \text{ p.u.}$$

*Again, analysis is exactly the same*

*Difference appear when we convert back to actual values*

$$V_L^{actual} = 0.859 \angle (-30.8^\circ) \times 27.6kV = 23.8 \angle (-30.8^\circ) kV$$


$$S_L^{actual} = 0.189 \angle 0^\circ \times 300MVA = 0.567 \angle 0^\circ MVA$$

$$S_G^{actual} = 0.22 \angle 30.8^\circ \times 300MVA = 0.66 \angle 30.8^\circ MVA$$

$$I_B^{Middle} = \frac{300MVA}{\sqrt{3} * 138kV} = 1250 A \text{ (*same currents*)}$$


$$I_{Middle}^{actual} = 0.22 \angle -30.8^\circ \times 1250 A = 275 \angle -30.8^\circ A$$

## Example 3

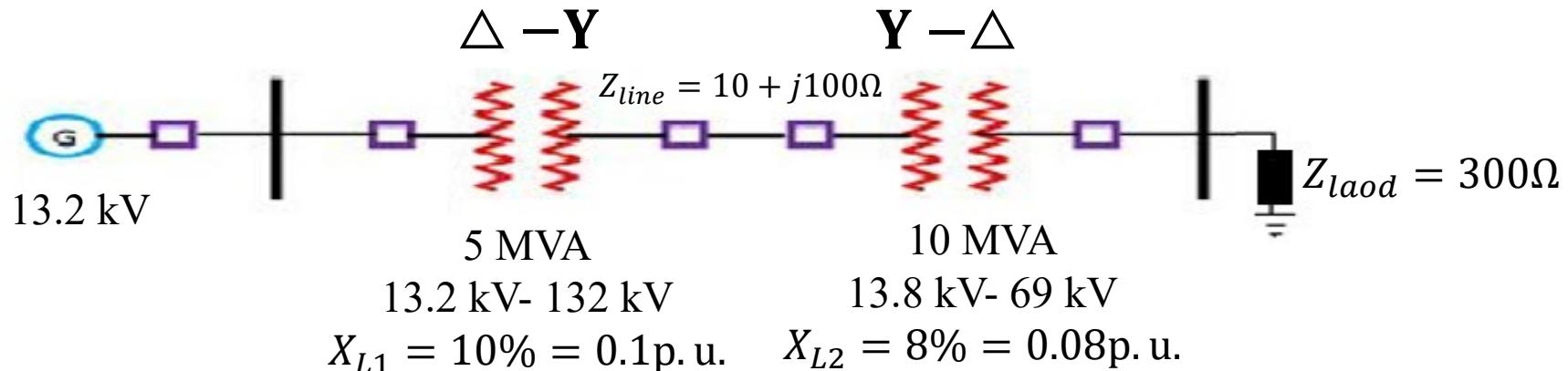

Q. Find the equivalent p. u values of each component.

## Example 3: Solution

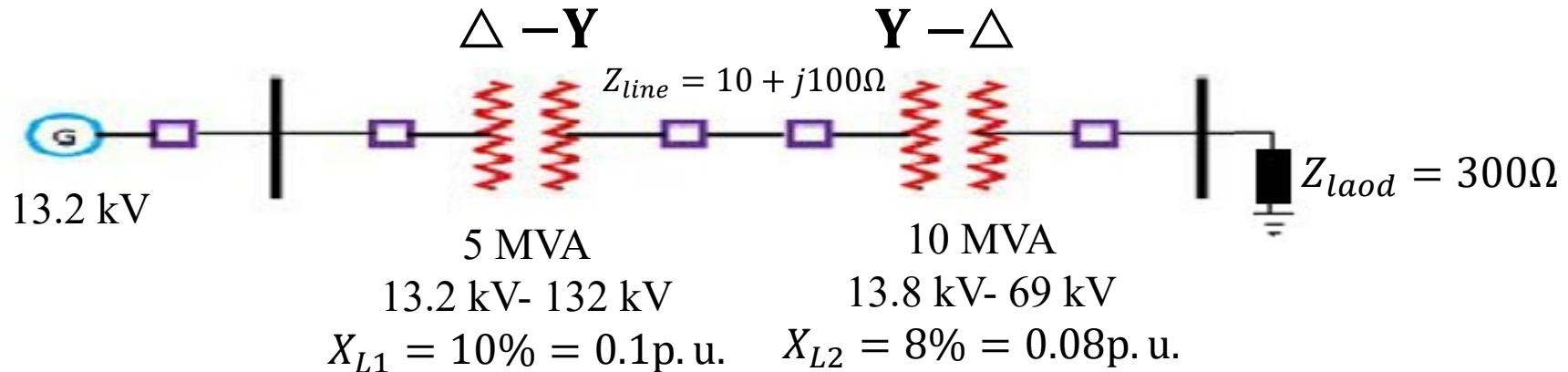


$$S_B^{3\phi} = 10 \text{ MVA}$$

$$V_{3B}^{\text{L-L}} = 69 \text{ kV}$$

$$V_{2B}^{\text{L-L}} = 138 \text{ kV}$$

$$V_{1B}^{\text{L-L}} = 138 \text{ kV} \times \frac{13.2\text{kV}}{132\text{kV}} = 13.8\text{kV}$$

## Example 3: Solution

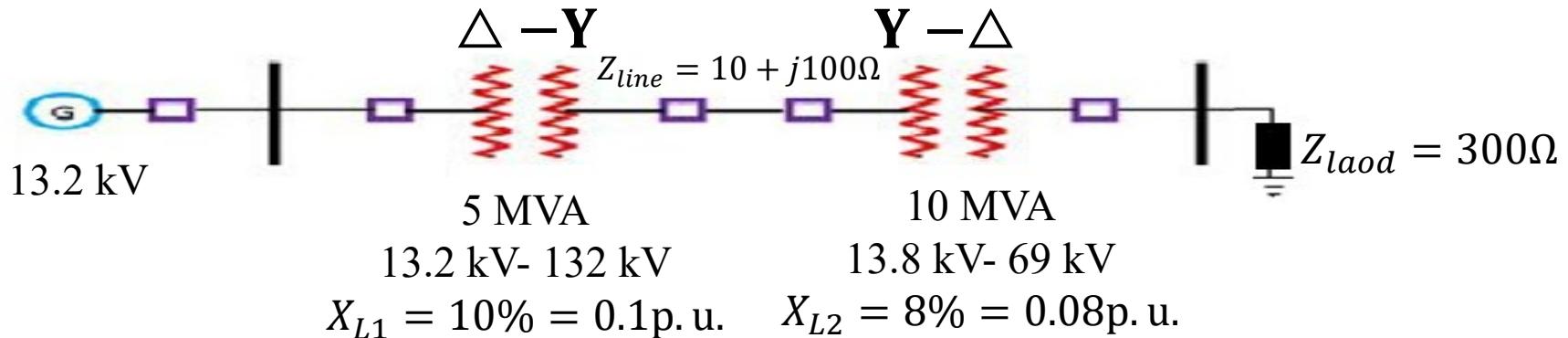

$$V_{3B}^{\text{L-L}} = 69 \text{ kV}$$

$$V_{2B}^{\text{L-L}} = 138 \text{ kV}$$


$$V_{1B}^{\text{L-L}} = 13.8 \text{ kV}$$

$$Z_{3B} = \frac{(V_{3B}^{\text{L-L}})^2}{S_B^{3\phi}} = \frac{69^2}{10} = 476\Omega$$

$$Z_{2B} = \frac{(V_{2B}^{\text{L-L}})^2}{S_B^{3\phi}} = \frac{138^2}{10} = 1904\Omega$$

$$Z_{1B} = \frac{(V_{1B}^{\text{L-L}})^2}{S_B^{3\phi}} = \frac{13.8^2}{10} = 19.04\Omega$$

## Example 3: Solution

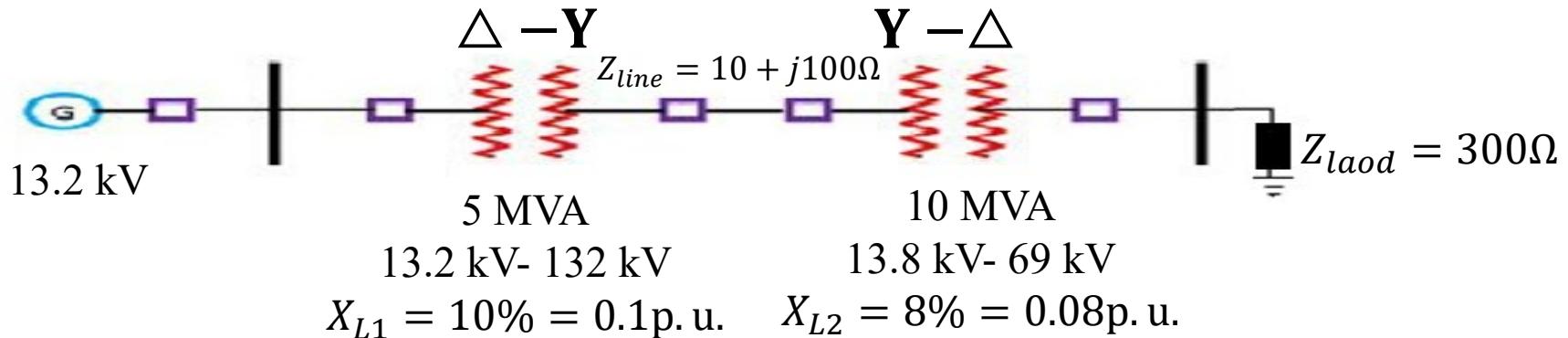

$$S_B^{3\phi} = 10 \text{ MVA}$$


$$V_{3B}^{\text{L-L}} = 69 \text{ kV} \quad V_{2B}^{\text{L-L}} = 138 \text{ kV} \quad V_{1B}^{\text{L-L}} = 13.8 \text{ kV}$$

$$Z_{3B} = \frac{(V_{3B}^{\text{L-L}})^2}{S_B^{3\phi}} = \frac{69^2}{10} = 476\Omega$$

$$Z_{2B} = \frac{(V_{2B}^{\text{L-L}})^2}{S_B^{3\phi}} = \frac{138^2}{10} = 1904\Omega$$

$$Z_{1B} = \frac{(V_{1B}^{\text{L-L}})^2}{S_B^{3\phi}} = \frac{13.8^2}{10} = 19.04\Omega$$

## Example 3: Solution

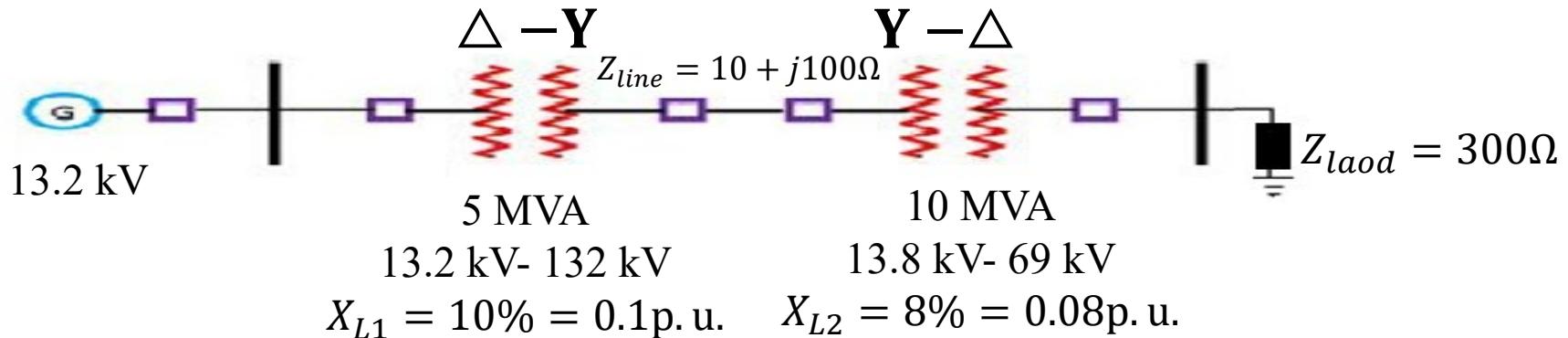


$$Z_{load} = \frac{350\Omega}{476\Omega} = 0.63 \text{ p.u.}$$

$$Z_{line} = \frac{10 + j100\Omega}{1904\Omega} = 0.005 + j0.05 \text{ p.u.}$$

$$E_s = \frac{13.2\text{kV}}{13.8 \text{ kV}} = 0.96 \text{ p.u.}$$


## Example 3: Solution

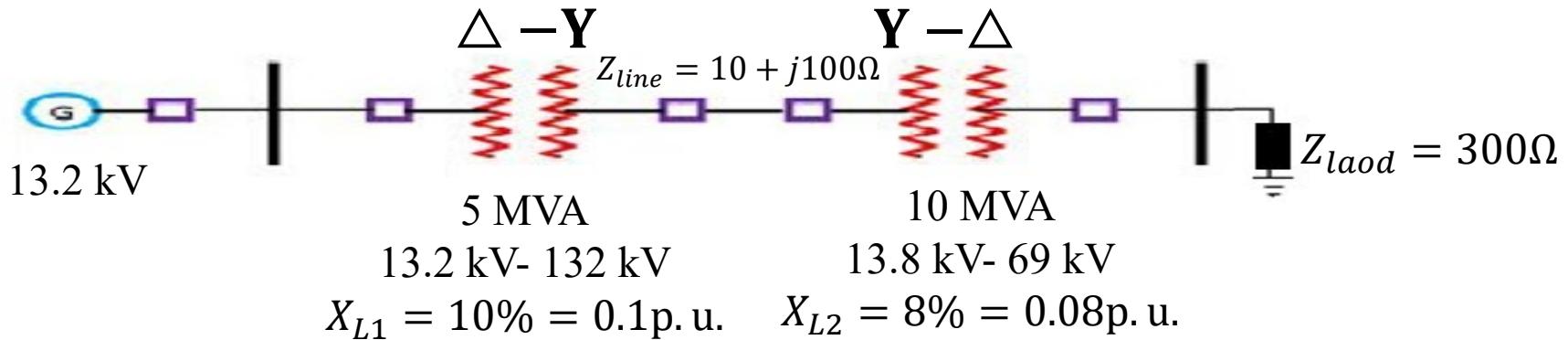

$$X_{L2} = \frac{0.08 \times \frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}}}{Z_{3B}} = \frac{0.08 \times \frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}}}{\frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}}} = 0.08$$

$$X_{L1} = \frac{0.1 \times \frac{(13.2\text{kV})^2}{5\text{ MVA}}}{Z_{1B}} = \frac{0.1 \times \frac{(13.2)^2}{5}}{\frac{(13.8)^2}{10}} = 0.183 \text{ p.u}$$

## Example 3: Solution

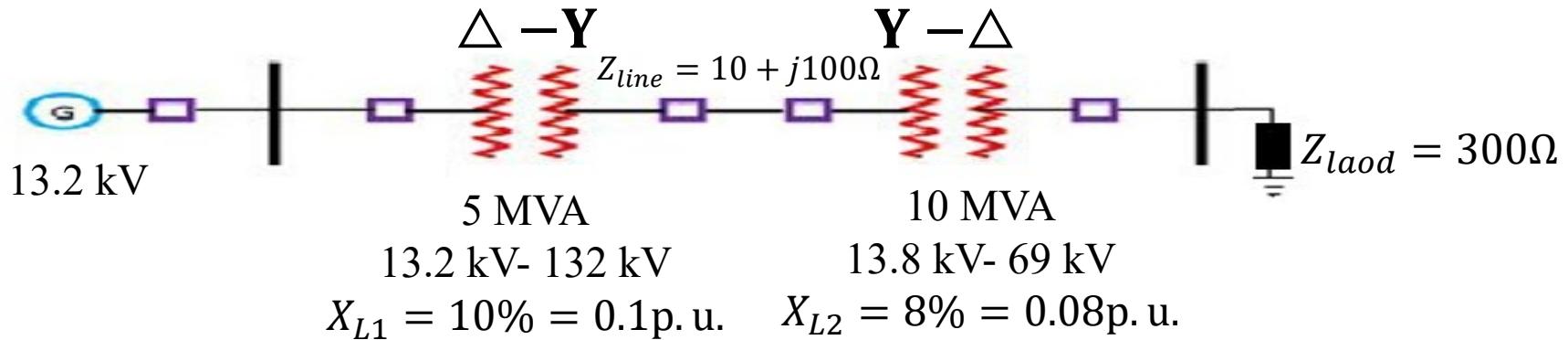

$$X_{L1} = \frac{0.1 \times \frac{(13.2\text{kV})^2}{5\text{ MVA}}}{Z_{1B}} = \frac{0.1 \times \frac{(13.2)^2}{5}}{\frac{(13.8)^2}{10}} = 0.183 \text{ p.u}$$

Alternatively, we can find  $X_{L1}$  as,

$$X_{L1} = \frac{0.1 \times \frac{(132\text{kV})^2}{5\text{ MVA}}}{Z_{2B}} = \frac{0.1 \times \frac{(132)^2}{5}}{\frac{(138)^2}{10}} = 0.183 \text{ p.u}$$

# Thank You!