

IOWA STATE UNIVERSITY

ECpE Department

EE 303 Energy Systems and Power Electronics

Power Electronics

GRA: Prashant Tiwari

Advisor: Dr. Zhaoyu Wang

1113 Coover Hall, Ames, IA



wzy@iastate.edu

IOWA STATE UNIVERSITY

DC – DC Converters

- Buck Converter (Step – Down Converter)
- Boost Converter (Step – Up Converter)
- Buck – Boost Converter (Step Up/Down Converter)

Buck Converter – Step Down Converter

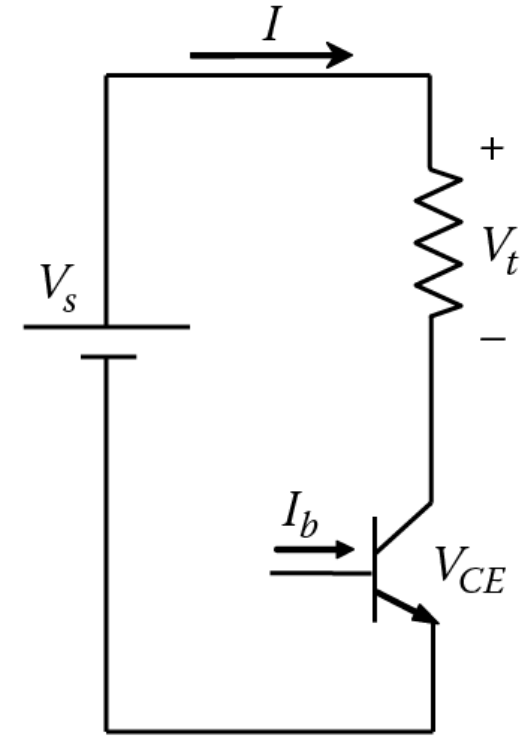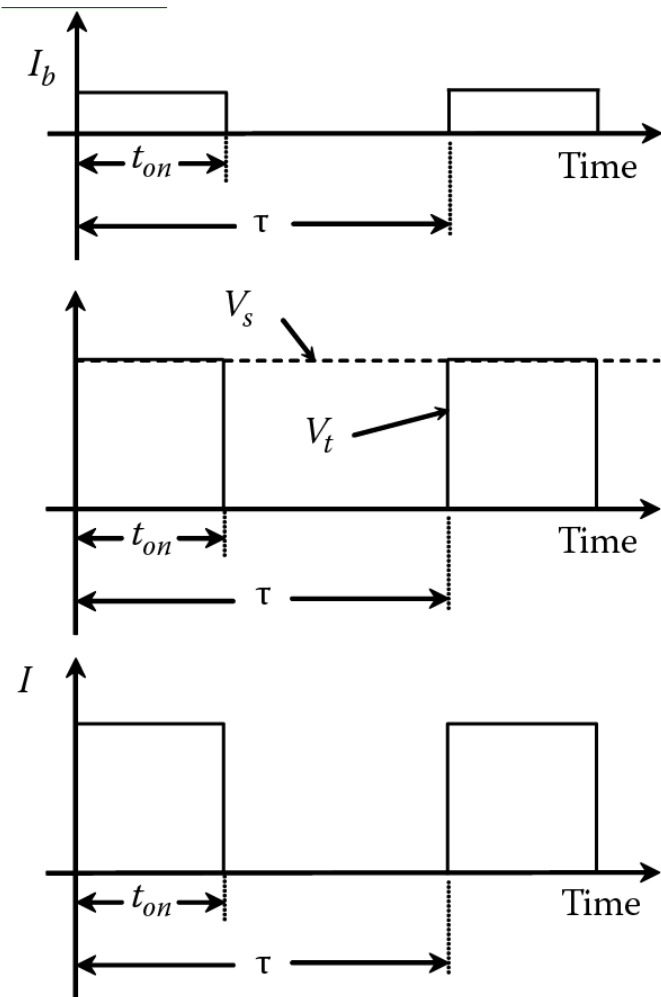


Contd...

$$V_{ave} = \frac{1}{\tau} \int_0^t V_s dt$$

$$= \frac{t_{on}}{\tau} \cdot V_s$$

$$k = \frac{t_{on}}{\tau} = \text{duty ratio}$$

$$V_{ave} = k \cdot V_s$$

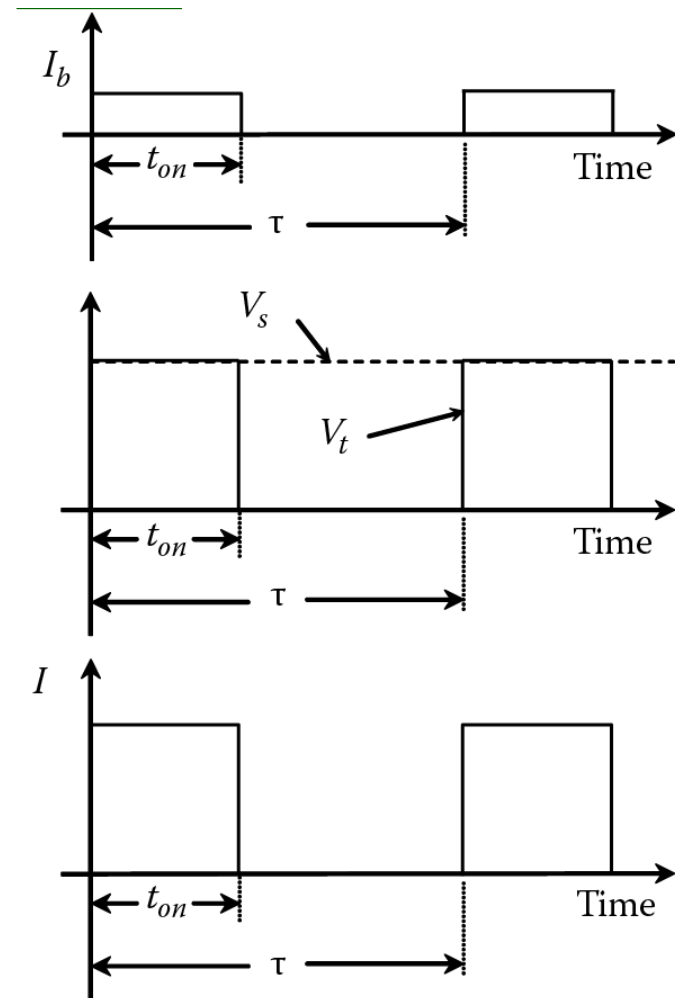

Example

The switching frequency of a chopper is 10 KHz, and the source voltage is 40 V. For an average load voltage of 20 V and a load resistance of 10 Ω , compute the following:

1. Duty ratio
2. Average current of the load
3. rms voltage across the load
4. Load power

Example

Solution

1. The duty ratio is

$$K = \frac{V_{\text{ave}}}{V_s} = \frac{20}{40} = 0.5$$

Before we compute the on-time, we need to compute the period:

$$\begin{aligned}\tau &= \frac{1}{f} = \frac{1}{10} = 0.1 \text{ ms} \\ t_{\text{on}} &= K\tau = 0.5 \times 0.1 = 0.05 \text{ ms}\end{aligned}$$

2. The average load current is

$$I_{\text{ave}} = \frac{V_{\text{ave}}}{R} = \frac{20}{10} = 2 \text{ A}$$

3. The rms voltage of the load can be computed using the standard formula for the rms quantity


$$V = \sqrt{\frac{1}{\tau} \int_0^{t_{\text{on}}} V_s^2 dt} = \sqrt{\frac{V_s^2}{\tau} t_{\text{on}}} = V_s \sqrt{\frac{t_{\text{on}}}{\tau}} = 28.28 \text{ V}$$

4. $P = \frac{V^2}{R} = \frac{28.28^2}{10} = 80 \text{ W}$



DC – DC Converters

- Buck Converter (Step – Down Converter)
- Boost Converter (Step – Up Converter)
- Buck – Boost Converter (Step Up/Down Converter)

Boost Converter

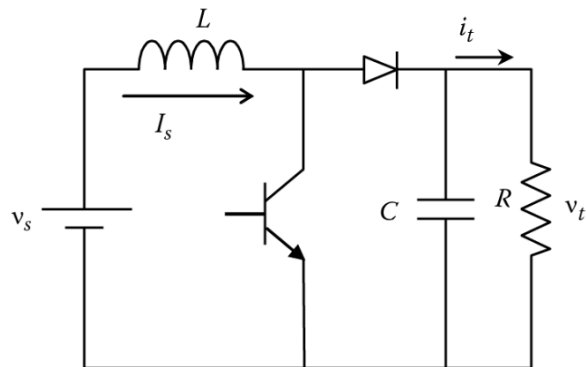

Filter reduces the voltage ripple

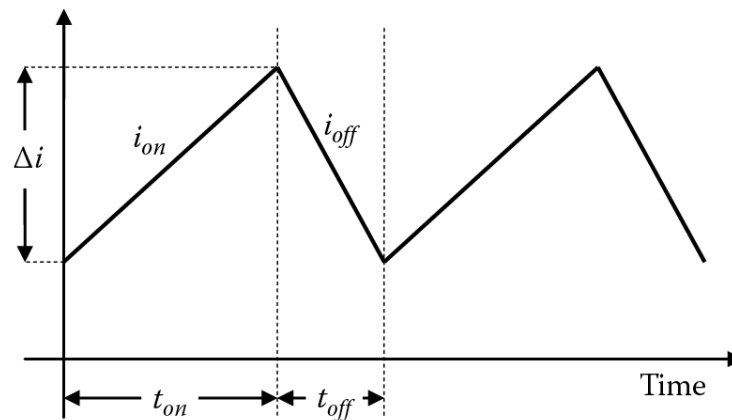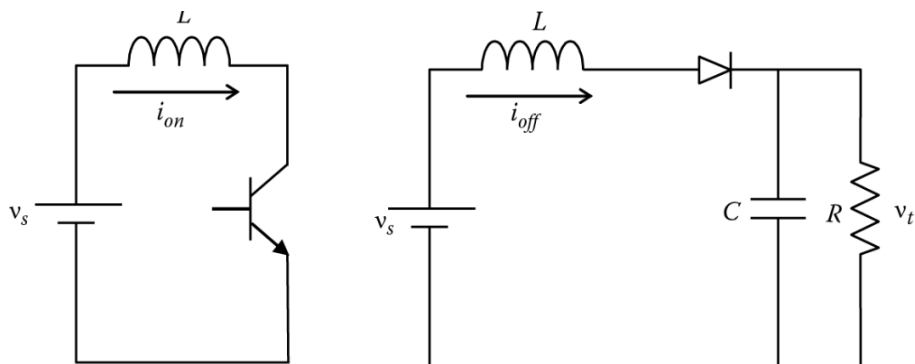

Waveform of boost converter.

Contd...

- When transistor is closed. (t_{on}, i_{on}), **charge inductor**

$$V_L = L \frac{di_{on}}{dt} = L \frac{\Delta i_{on}}{t_{on}}$$

where Δi_{on} is the change in the current during the period t_{on} . Since the voltage across the inductor is equal to the source voltage when the transistor is closed.

$$V_s = L \frac{\Delta i_{on}}{t_{on}}$$

- When transistor is open. (t_{off}, i_{off}), **discharge inductor**

$$V_t = V_s + V_L = V_s + L \frac{di_{off}}{dt} = V_s + L \frac{\Delta i_{off}}{t_{off}}$$

Contd...




$$V_t = V_s + V_L = V_s + L \frac{di_{off}}{dt} = V_s + L \frac{\Delta i_{off}}{t_{off}}$$

$$V_t = V_s + V_s \frac{t_{on}}{\Delta i_{on}} \cdot \frac{\Delta i_{off}}{t_{off}}$$

$$\Delta i_{on} = \Delta i_{off}$$

$$V_t = V_s + V_s \frac{t_{on}}{t_{off}} = V_s \left(1 + \frac{t_{on}}{t_{off}}\right)$$

Buck – Boost Converter

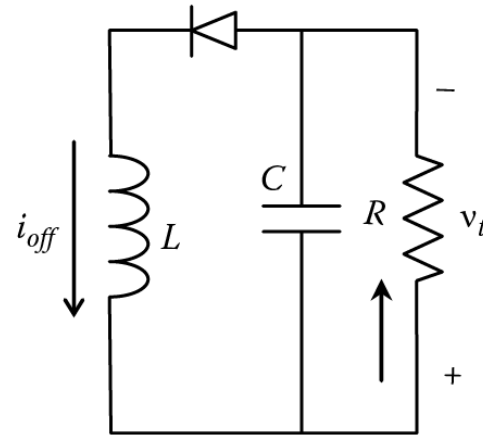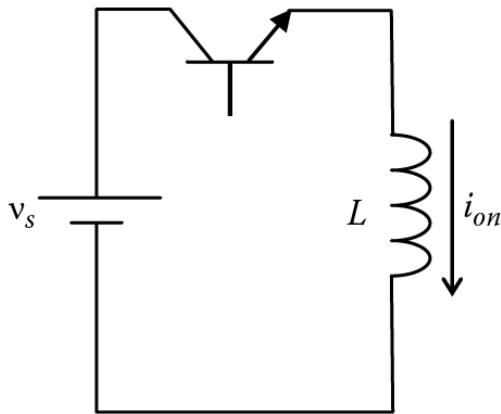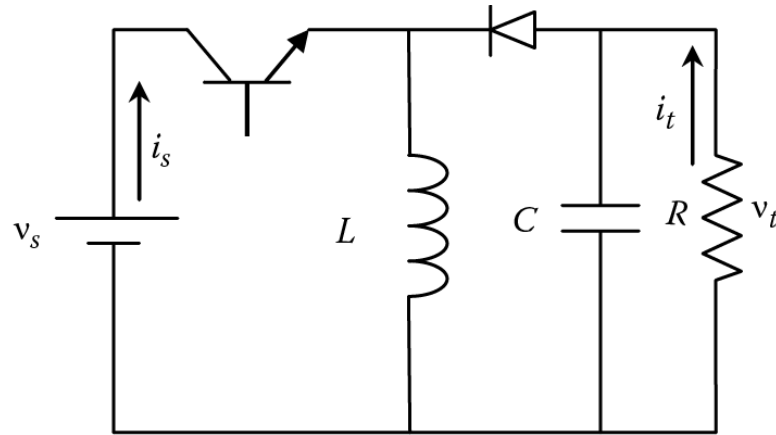

Contd...


- When transistor is closed. (t_{on}, i_{on})

$$V_L = L \frac{di_{on}}{dt} = L \frac{\Delta i_{on}}{t_{on}}$$


$$V_s = V_L = L \frac{\Delta i_{on}}{t_{on}}$$

- When transistor is open. (t_{off}, i_{off})

$$V_L = \frac{\Delta i_{off}}{t_{off}}$$

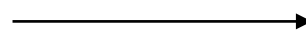

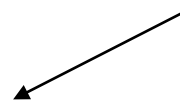
$$V_t = V_L = L \frac{\Delta i_{off}}{t_{off}}$$



$$V_t = V_s \frac{t_{on}}{\Delta i_{on}} \cdot \frac{\Delta i_{off}}{t_{off}}$$

$$(\Delta i_{on} = \Delta i_{off})$$

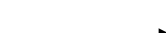

$$V_t = V_s \frac{t_{on}}{t_{off}}$$

Example

A buck–boost converter with an input voltage of 20 V is used to regulate the voltage across a 10 Ω load. The switching frequency of the transistor is 5 kHz. Compute the following:

- On-time of the transistor to maintain the output voltage at 10 V

Example

A buck–boost converter with an input voltage of 20 V is used to regulate the voltage across a 10 Ω load. The switching frequency of the transistor is 5 kHz. Compute the following:

- On-time of the transistor to maintain the output voltage at 10 V

Solution,

The period can be computed from the switching frequency f

- $\tau = \frac{1}{f} = \frac{1}{5} = 0.2 \text{ ms}$

- $V_t = V_s \frac{t_{on}}{\Delta i_{on}}$


$$\frac{t_{on}}{t_{off}} = \frac{V_t}{V_s} = \frac{10}{20} = 0.5$$

$$t_{off} + t_{on} = \tau$$


$$t_{on} = 0.0667 \text{ ms}$$

DC-AC Inverter (H- Bridge Circuit)



- Most of the inverter consists of simple H-Bridge arrangement. The circuit is an implementation of a single-phase H-Bridge circuit using Insulated Gate Bipolar Transistors (IGBT).
- The IGBT act as a switch in the above circuit.
- When a signal is applied to the gate, they turn on and when the signal is removed, they turn off. By closing Q1 and Q4, a positive DC supply is applied to the load.
- The Q3, and Q3 will result in a negative *DC* supply across the load.
- Then the control circuits are used to generate the necessary gate signals to produce the required PWM waveform.
- It is necessary to avoid short circuits. This happens by closing both Q1 and Q2 at the same time. To avoid this, it is necessary to turn off one set of IGBT before turning on the next.
- The Diodes provide a necessary path for inductive current in order to limit potential voltage build-up during the transition period. The capacitor provides smoothing to even out any variation in the DC supply.

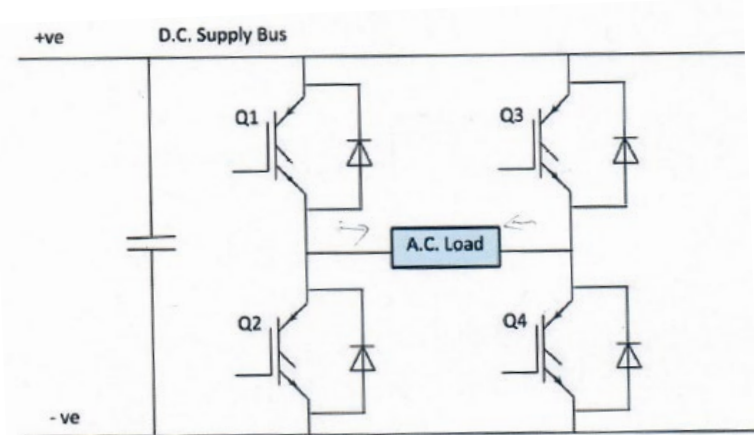


Contd...

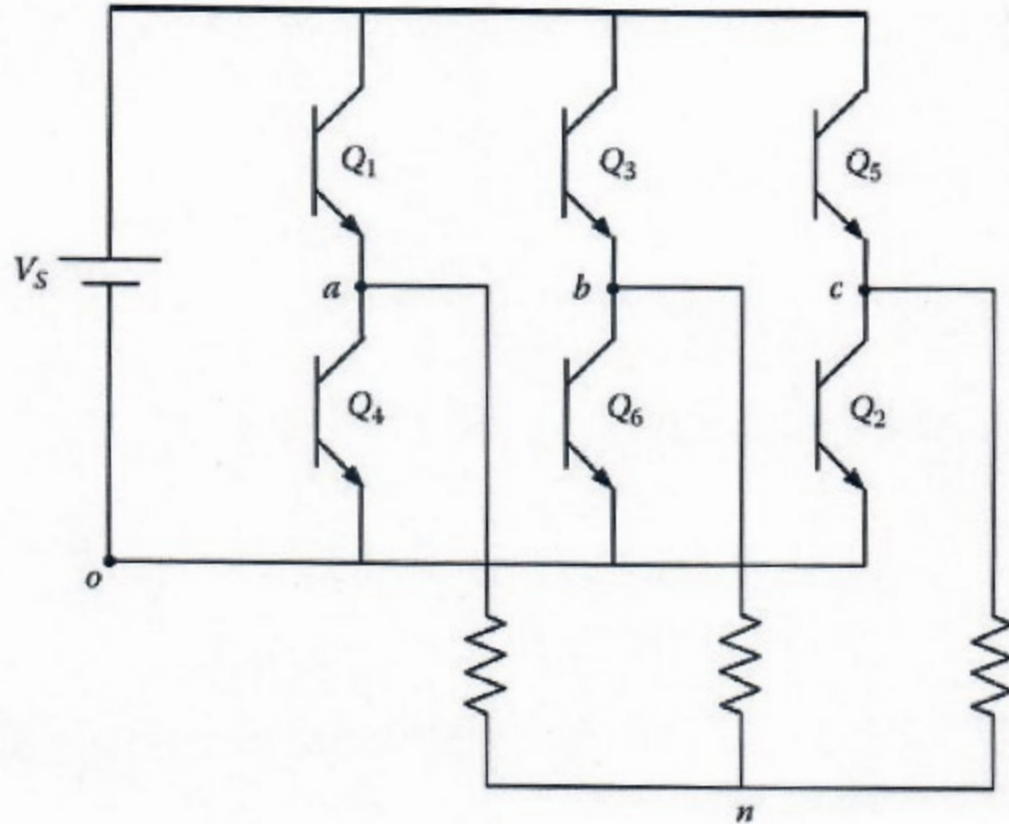

Contd...

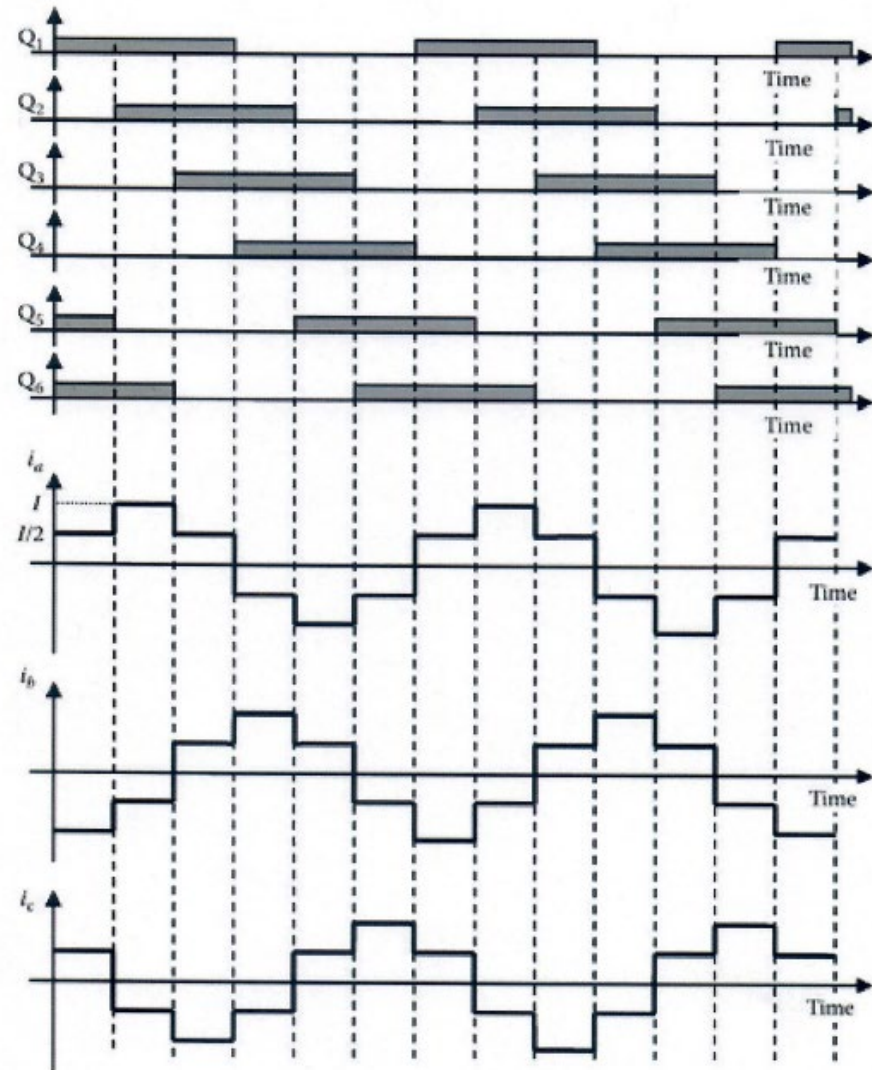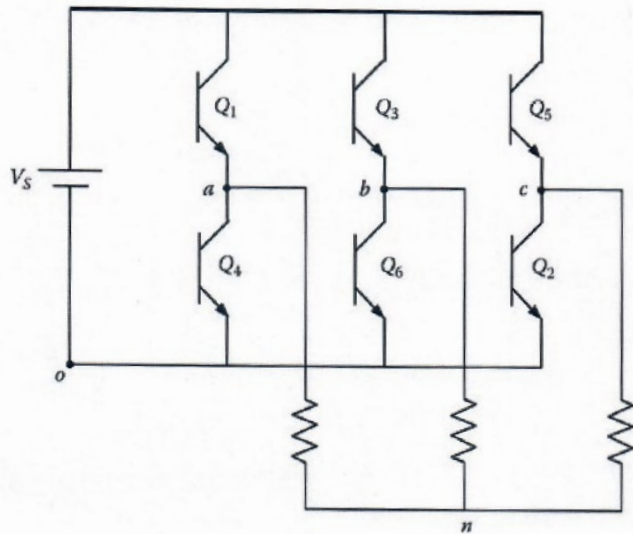

Contd...

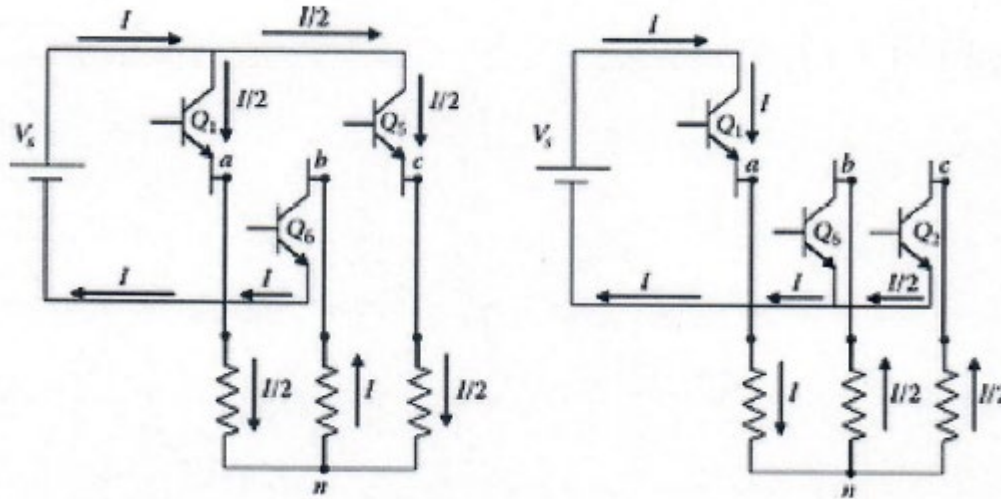

Thank You!